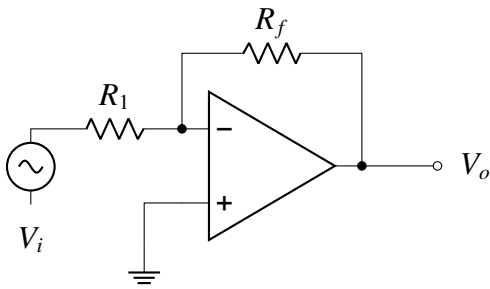



# Operational Amplifier (Op-Amp)

## Op-Amp: Single Ended Mode




Inverting Amplifier


$$A_v = -\frac{R_f}{R_1}$$

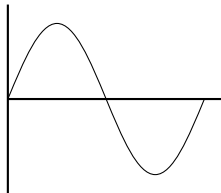

Analog Input

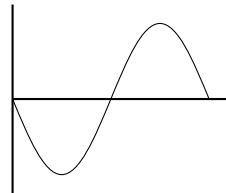


Analog Output

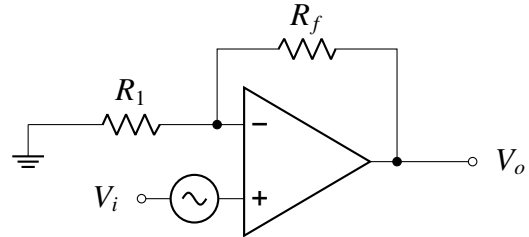


Non-Inverting Amplifier

$$A_v = 1 + \frac{R_f}{R_1}$$

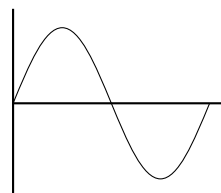


Analog Input

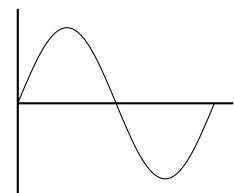

Analog Output

## Op-Amp: Differential Mode

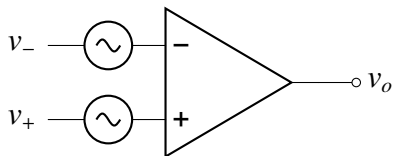

$$v_o = A_v v_d$$


When  $v_+ > v_-$ ,  $\therefore v_d = v_+ - v_-$

$\Rightarrow$  (Non-inverting amplifier)

When  $v_- > v_+$ ,  $\therefore v_d = v_- - v_+$

$\Rightarrow$  (Inverting amplifier)

## Op-Amp: Voltage Follower

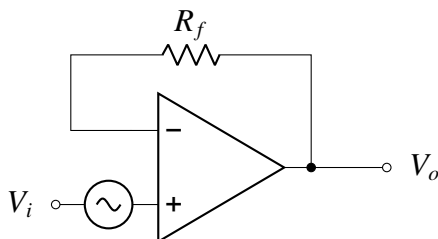


For voltage follower, Gain,  $A_v = 1$

$$\therefore v_o = A_v v_i = 1 \cdot v_i = v_i$$

$$\therefore v_o = v_i$$


## Op-Amp: Adder/Summer

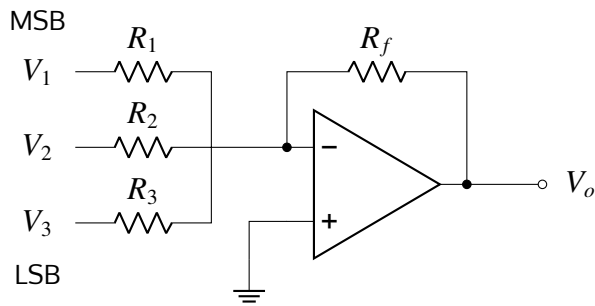

$$V_o = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3\right)$$

$$= -R_f\left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}\right)$$


## Op-Amp: Binary Weighted DAC

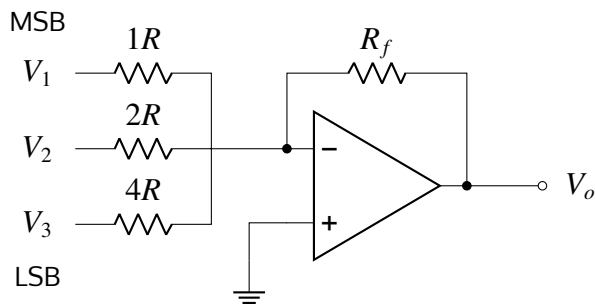

$$V_o = -\left(\frac{R_f}{1R}V_1 + \frac{R_f}{2R}V_2 + \frac{R_f}{4R}V_3\right)$$

$$= -\frac{R_f}{R}\left(\frac{V_1}{1} + \frac{V_2}{2} + \frac{V_3}{4}\right)$$

## Virtual Ground

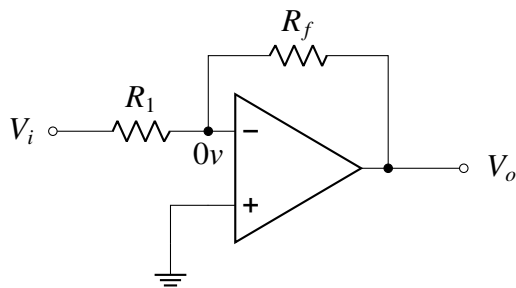


Let  $A_v = \infty$ , then  $(v_1 - v_2) = \frac{V_{out}}{A} = \frac{V_{out}}{\infty} = 0 \therefore v_1 = v_2$

If any one is connected to the ground, another one is also 0V


## An ideal op-amp characteristics

voltage gain	$\infty$
input impedance	$\infty$
CMRR	$\infty$
slew rate	$\infty$
Bandwidth	$\infty$
output impedance	0
input offset voltage	0
input offset current	0


## Op-Amp: Clipper Circuit

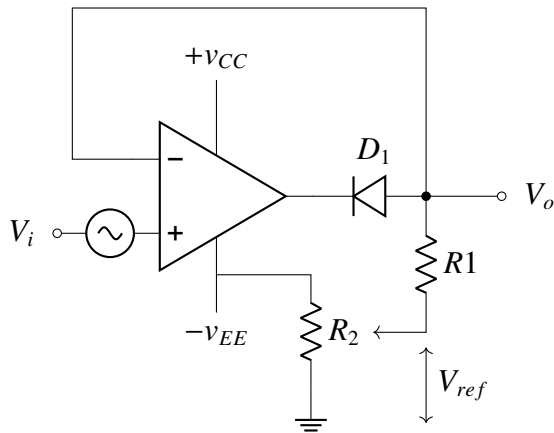


Positive Clipper

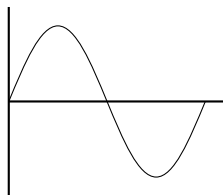


Analog Input

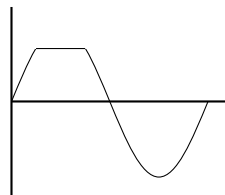


Analog Output

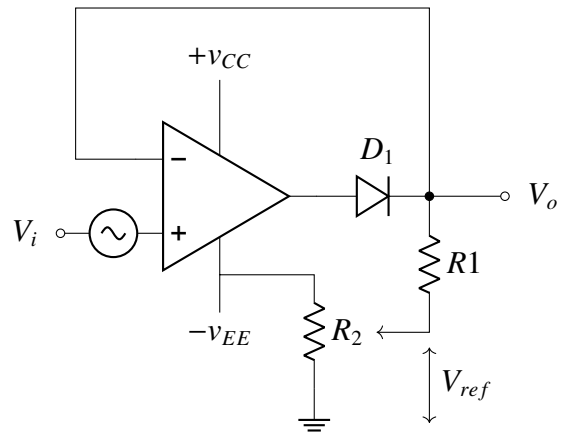

Negative Clipper

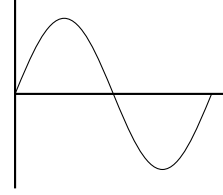


Analog Input

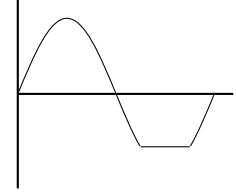


Analog Output


## Op-Amp: Half Wave Rectifier

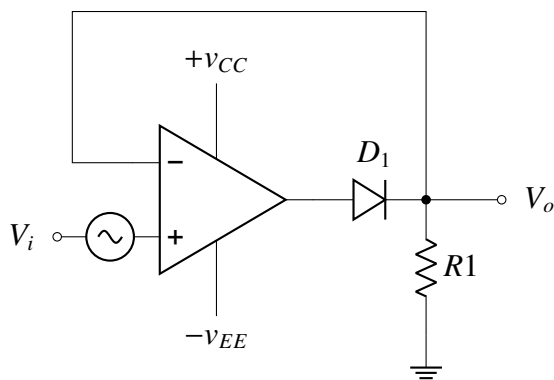


Positive Half Wave Rectifier

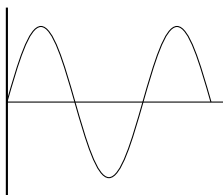


Analog Input

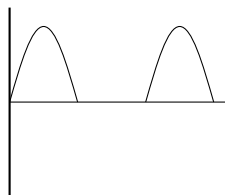


Analog Output

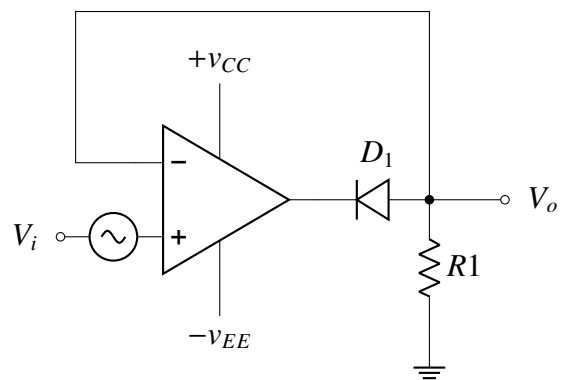

Negative Half Wave Rectifier

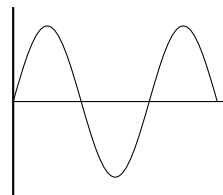


Analog Input

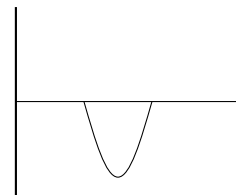


Analog Output

## Op-Amp: Clamper Circuit

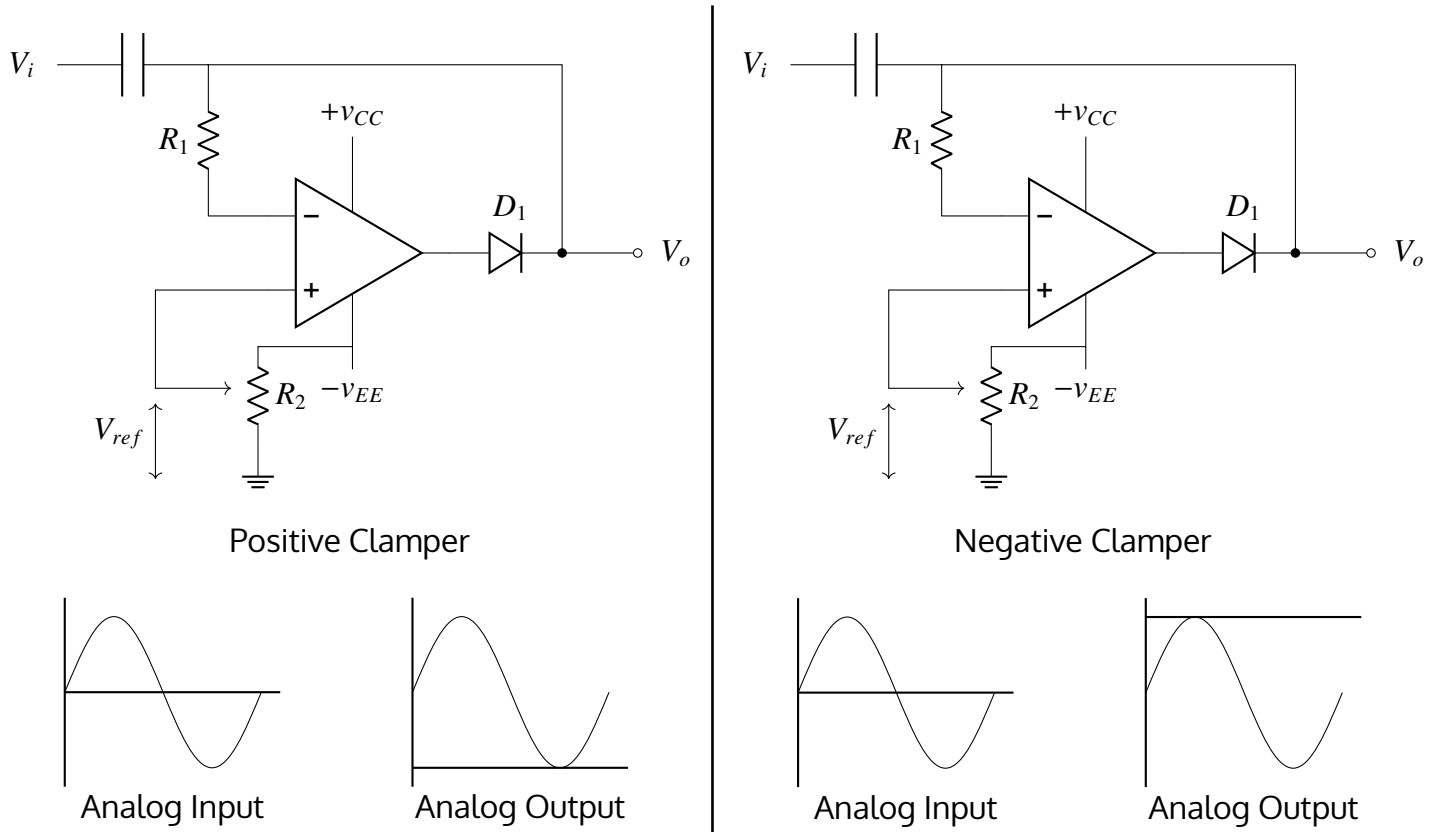
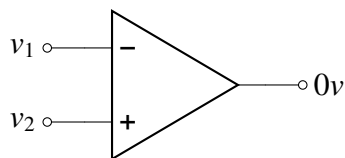
## Op-Amp: Common Mode

When two input signals voltages of same phase, frequency and magnitude are applied to both inputs, they tend to cancel each other resulting in a zero-output voltage. This action is called common mode rejection.



### Common Mode Rejection Ratio (CMRR)

Unwanted signals or noise appearing with same polarity on both lines of input are common mode signals and are cancelled by the op-amp. The measure of the op-amp's ability to reject common mode signals is expressed in terms of common mode rejection ratio (CMRR). It is defined as

$$CMRR = \frac{A_d}{A_c}$$


### Maximum Output Voltage Swing

The output voltage never exceeds the DC voltage supply ( $-V$  to  $+V$ ) of the Op-Amp.

## Flash ADC: 3 bit

**Components of Flash ADC:** Structure of Flash ADC consist three major components –

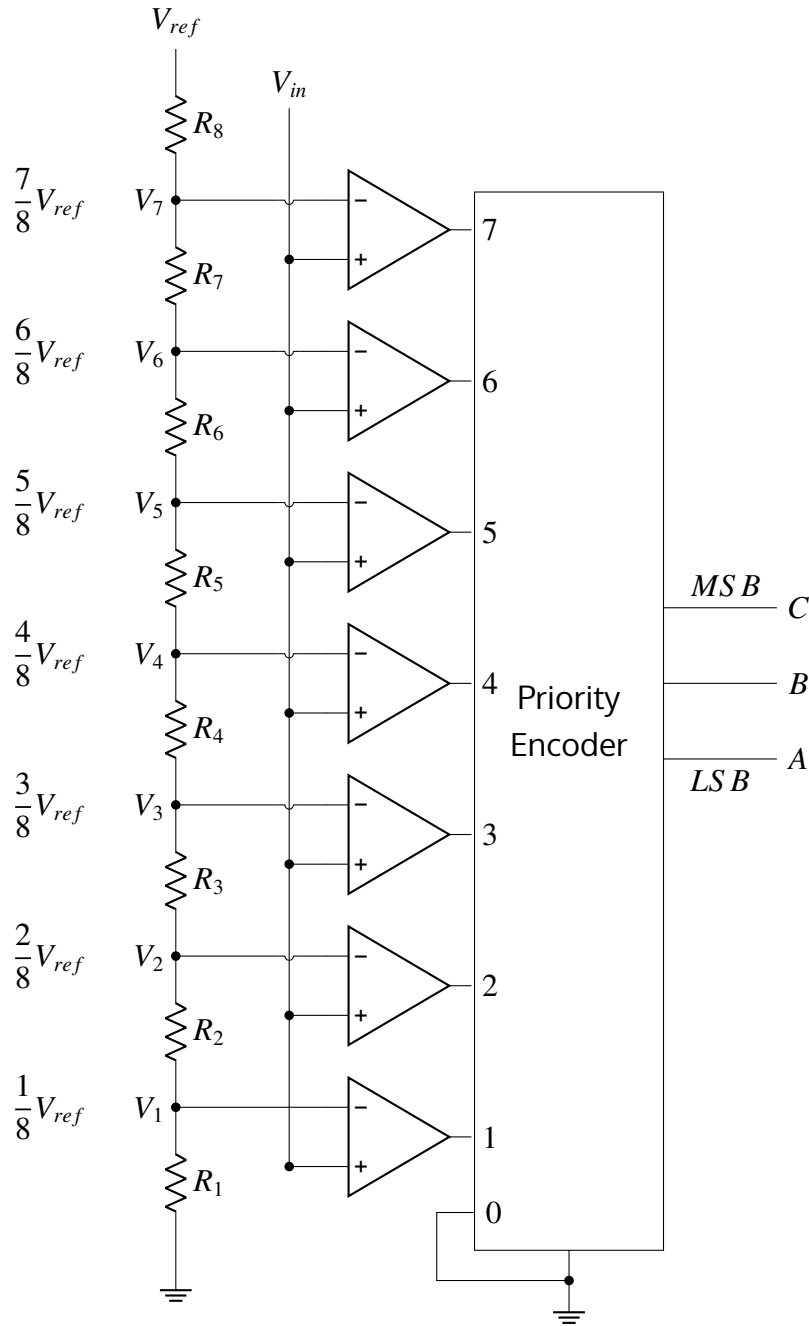1. High Speed Comparator [ $2^n - 1$ ]
2. Resistive voltage divider Network [ $2^n$ ]
3. Priority Encoder [1]



## Op-Amp: Extra Terms

**Input Offset Voltage:** The input offset voltage ( $V_{io}$ ) is defined as the voltage that must be applied between the two input terminals of the op amp to obtain zero volts at the output.

**Input Bias Current:** Ideally no current flows into the input terminals of op-amp. But in practice, a small amount of current flows into the input terminals. These currents are called bias current.

**Input Offset Current:** The difference between these two input bias currents are called input offset current.

**Input Impedance:** The input impedance in the differential mode is the total resistance between inverting and noninverting inputs.

**Output Impedance:** The output impedance is the resistance viewed from the output terminal of the op-amp.

**Slew rate:** The slew rate is defined as the maximum rate of output voltage change per unit time.

$$\text{Slew rate} = \frac{\Delta V_{out}}{\Delta t}$$